

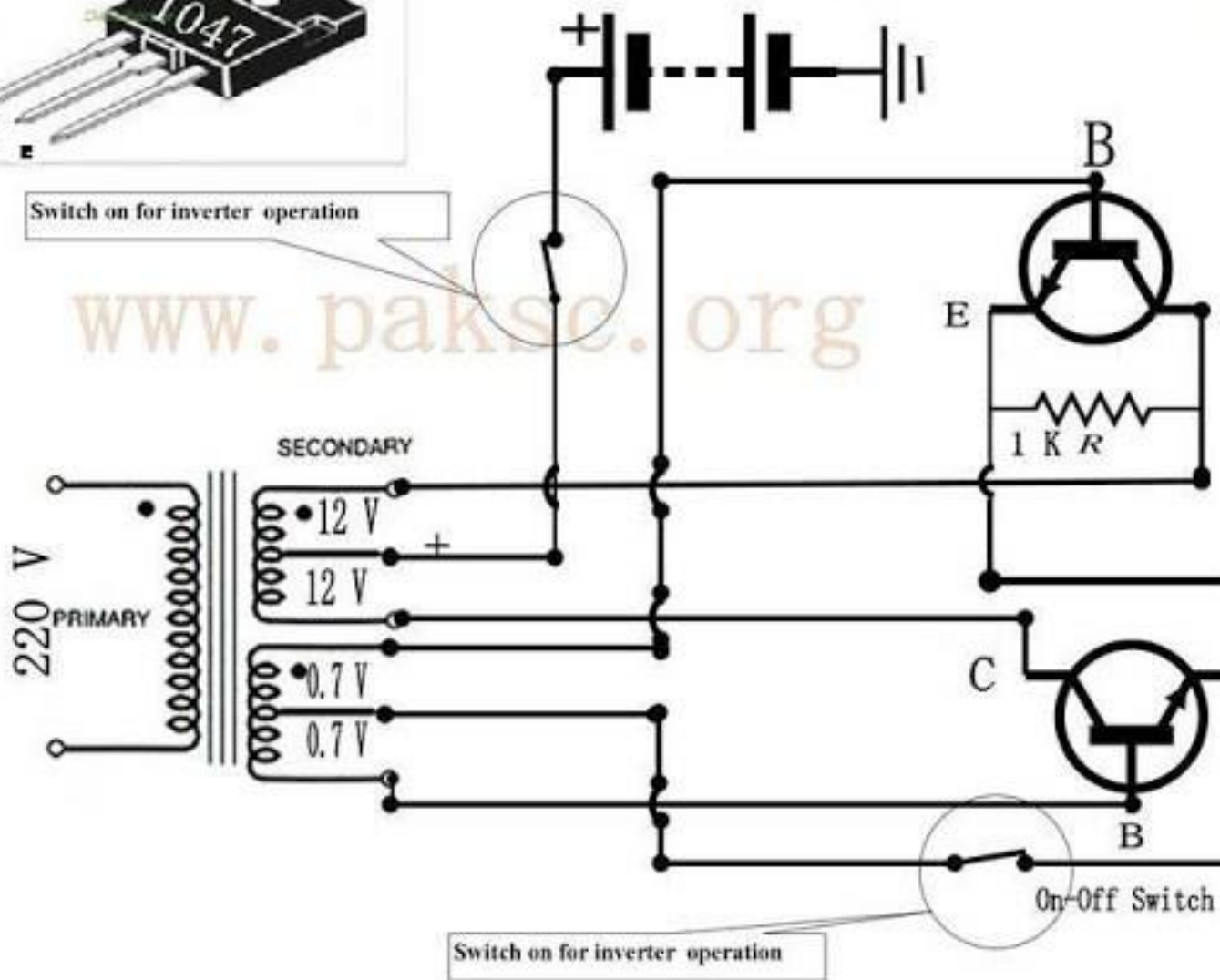


Switch on for inverter operation

inverter circuit diagram for inverter op

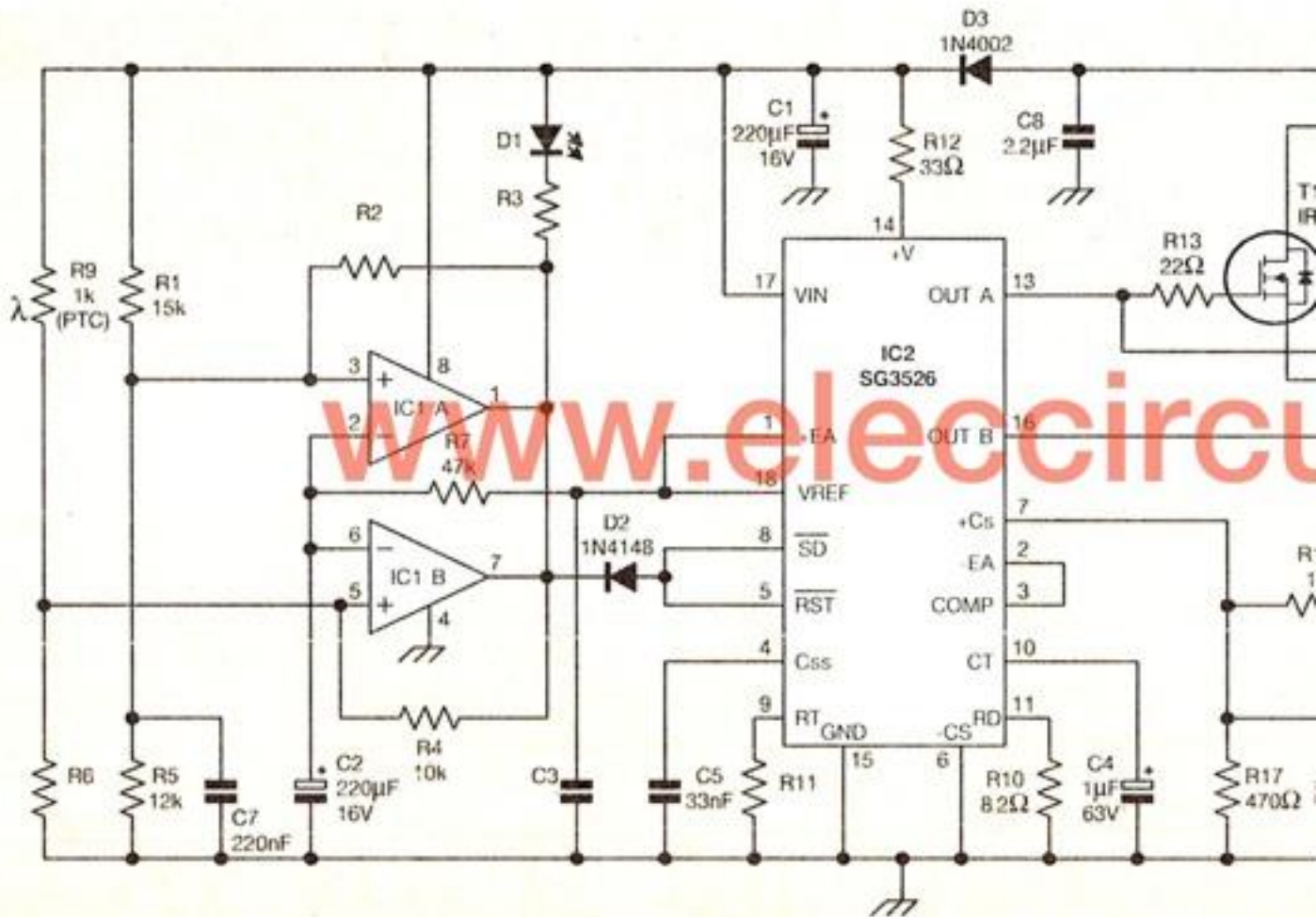

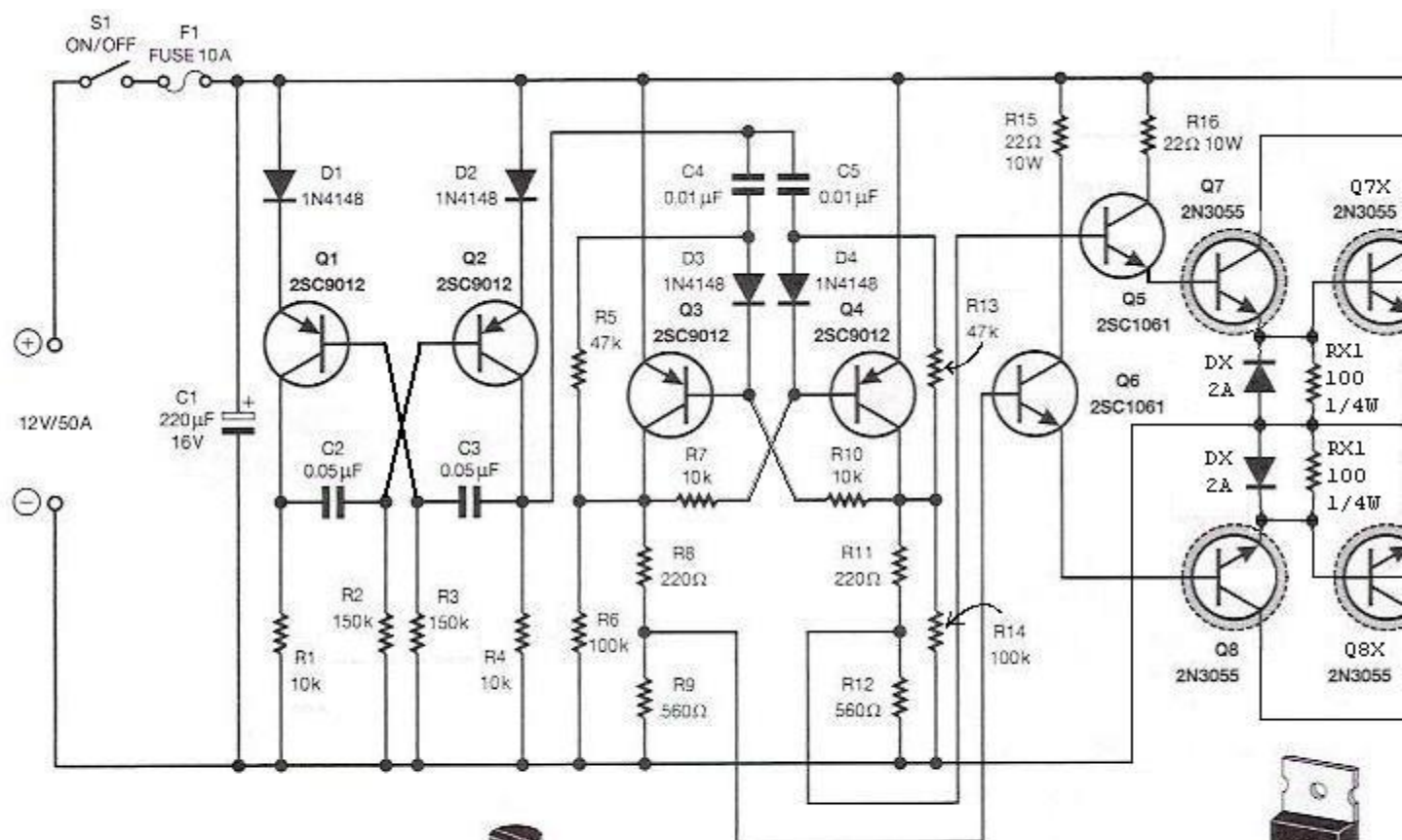




Q1-Q4





Q7,Q8

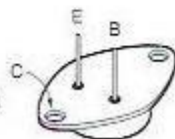

Q5,Q6



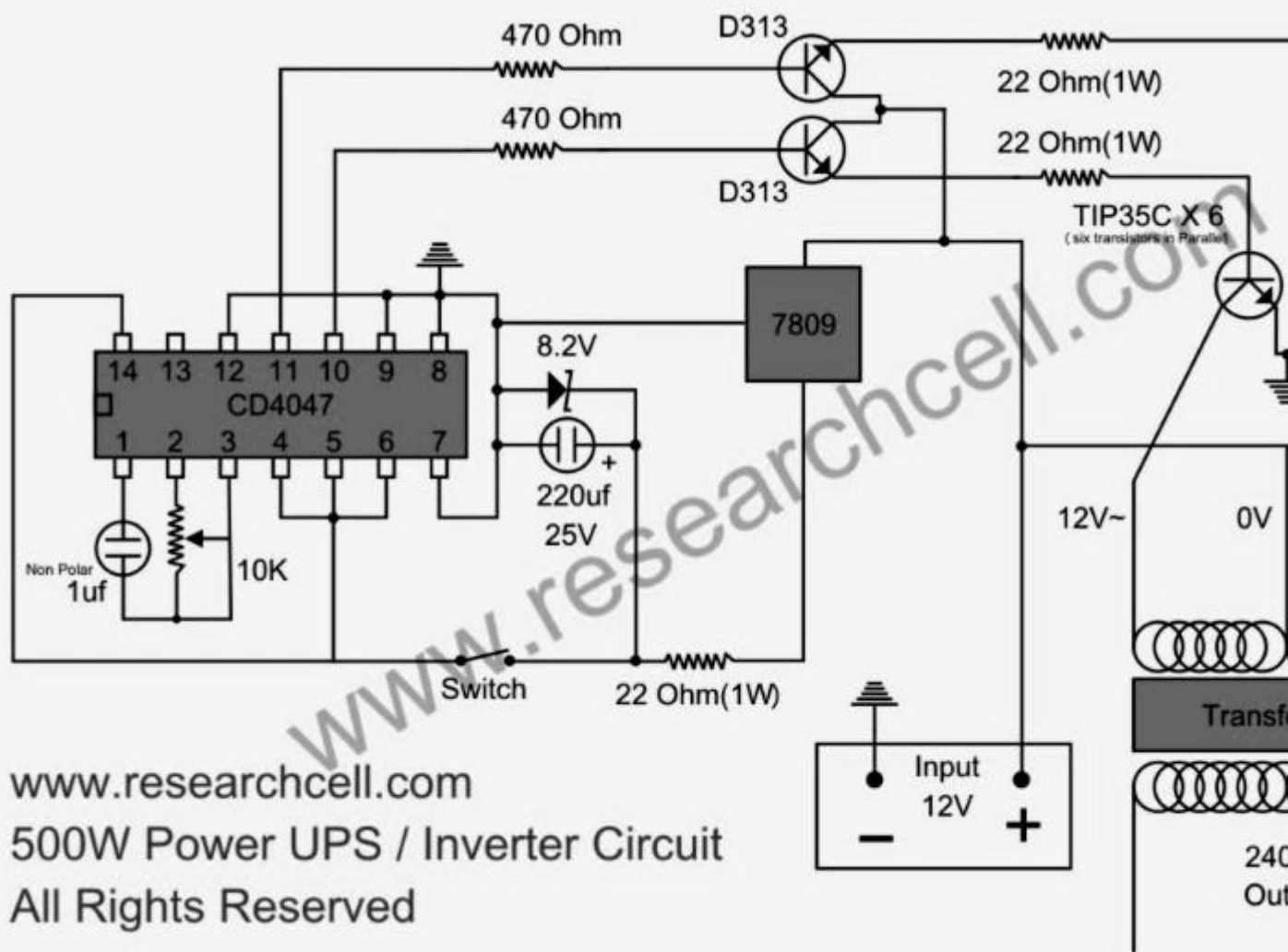

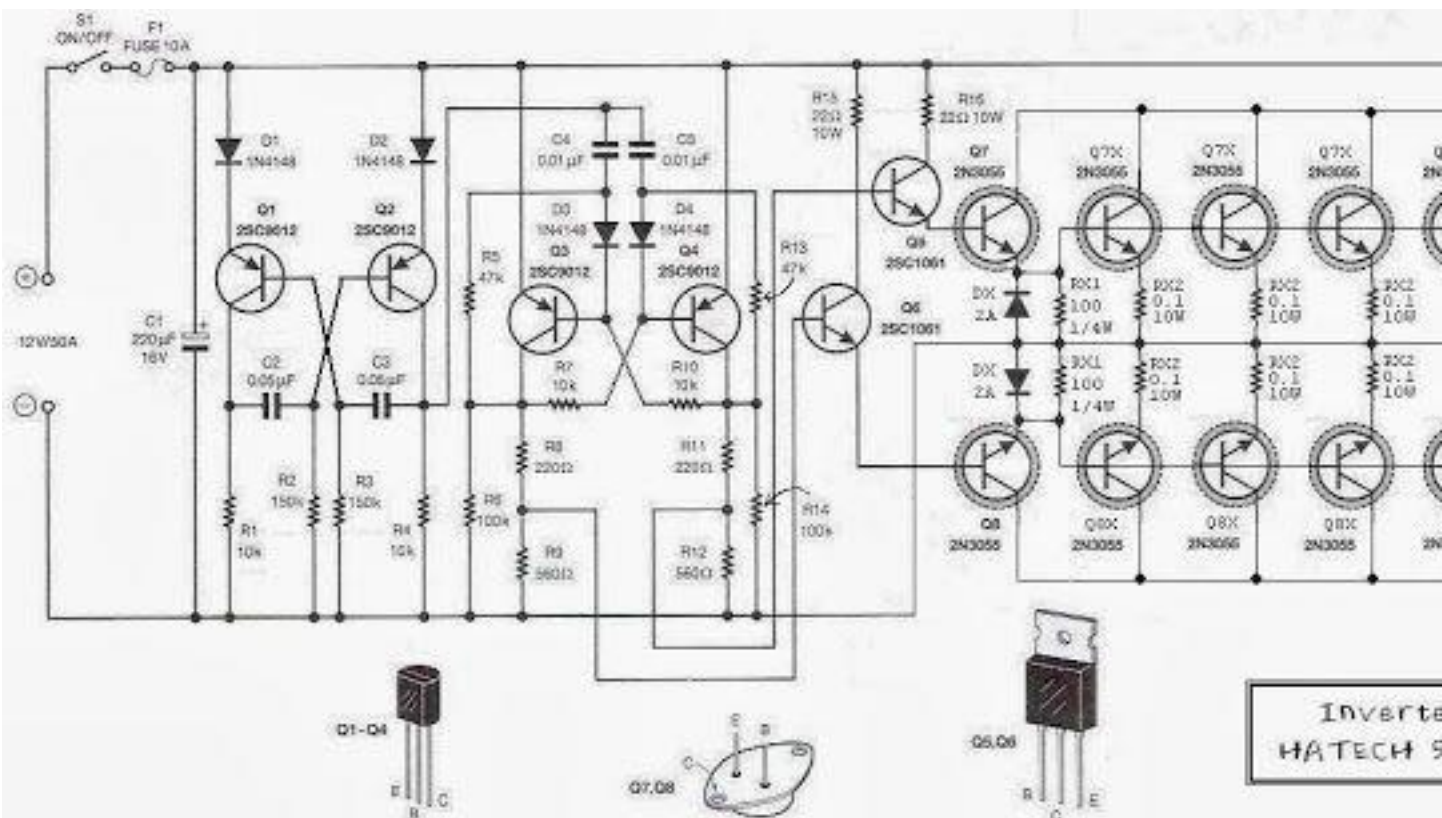

## Cheap 500W Inverter Circuit

+12V DC

T1= 12-0-1

